

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA

(An Autonomous Institute Affiliated to AKTU, Lucknow)

B.Tech

SEM: I - THEORY EXAMINATION (2024 - 2025)

Subject: Basic Electrical and Electronics Engineering

Time: 3 Hours

Max. Marks: 100

General Instructions:*IMP: Verify that you have received the question paper with the correct course, code, branch etc.**1. This Question paper comprises of three Sections -A, B, & C. It consists of Multiple Choice Questions (MCQ's) & Subjective type questions.**2. Maximum marks for each question are indicated on right -hand side of each question.**3. Illustrate your answers with neat sketches wherever necessary.**4. Assume suitable data if necessary.**5. Preferably, write the answers in sequential order.**6. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.***SECTION-A**

20

1. Attempt all parts:-

- 1-a. The internal voltage drop of a voltage source..... (CO1,K1) 1
- (a) Is independent of load current supplied
- (b) Depends upon internal resistance of the source
- (c) Does not influence the terminal voltage
- (d) Does affect the emf of the source
- 1-b. An electric circuit contains (CO1,K1) 1
- (a) active elements only
- (b) passive elements only
- (c) both active and passive elements
- (d) none of the above
- 1-c. In case of Inductive circuit, Frequency is _____ Proportional to the Current.(CO2,K1) 1
- (a) Directly
- (b) Inversely
- (c) No effect
- (d) None of the above
- 1-d. Average value of a sinusoidal alternating signal is _____for a full cycle.(CO2,K1) 1
- (a) Infinite

- (b) Maximum
 - (c) Minimum
 - (d) Zero
- 1-e. Earth leakage circuit breaker is also known as...(CO3,K1) 1
- (a) Residual current circuit breaker
 - (b) Miniature case circuit breaker
 - (c) oil control breaker
 - (d) Moulded circuit breaker
- 1-f. Purpose of Backup Protection is-(CO3,K1) 1
- (a) To guard against failure of primary
 - (b) To increase the speed
 - (c) To leave no blind spot
 - (d) None of the above
- 1-g. The efficiency of the full wave rectifiers is _____(CO4,K1) 1
- (a) 1
 - (b) 0.2224
 - (c) 0.812
 - (d) 0.742
- 1-h. The clipper circuit are used for.....(CO4,K1) 1
- (a) Rectification
 - (b) Removal of a part from the applied waveform
 - (c) Shifting of DC level
 - (d) None of these
- 1-i. CMRR value indicates the capability to reject (CO5,K1) 1
- (a) Power supply variation
 - (b) Difference of signal
 - (c) Common mode signal
 - (d) None of these
- 1-j. Basic building blocks of digital multimeter are _____. (CO5,K1) 1
- (a) oscillator, amplifier
 - (b) diode, op amp
 - (c) rectifier, schmitt trigger
 - (d) A/D, attenuator, counter

2. Attempt all parts:-

- 2.a. What do you mean by constant voltage source? Name some of them. (CO1,K1) 2
- 2.b. The polar form of the following waveform, $V_1 = 16 \sin (wt + 35^\circ) \text{ V}$, $V_2 = 32 \sin (wt - 55^\circ) \text{ V}$ is (CO2,K1) 2
- 2.c. What are the two components of no load current in a transformer?(CO3,K1) 2


- 2.d. Explain the Intrinsic and Extrinsic semiconductors.(CO4,K1) 2
- 2.e. Define the slew rate of Op-Amp. (CO5,K1) 2

SECTION-B


30

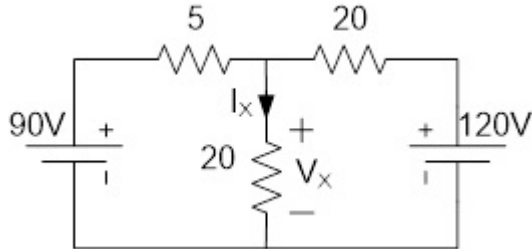3. Answer any five of the following:-

- 3-a. Find the current I_x and V_x in the circuit using Norton' Theorem. (CO1,K2) 6



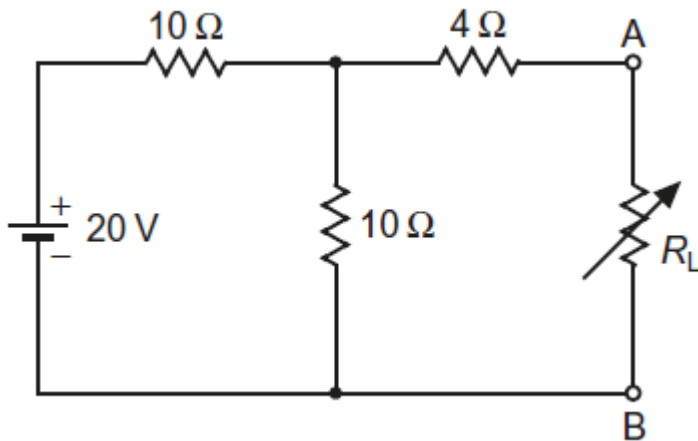- 3-b. In the network shown in Figure , determine the value of load resistance load resistance to give maximum power transfer and the power delivered to the load. (CO1) 6




- 3-c. Derive the equation of resonant circuit in parallel resonance. (CO2) 6
- 3-d. Find the relationships between line current and phase current in a delta connected three phase system (CO2) 6
- 3.e. Expalin the difference between ELCB and MCCB.(CO3) 6
- 3.f. Explain the Liquid Crystal Display (LCD) with neat diagram.(CO4) 6
- 3.g. What is role of sensors in IoT? List the types of sensors used in IoT.(CO5) 6

SECTION-C


50

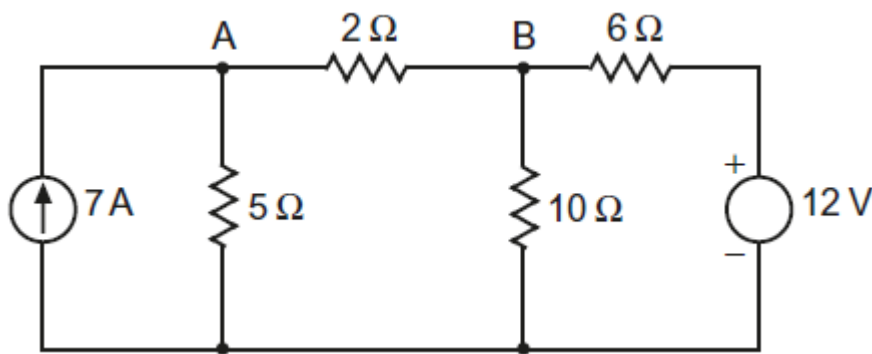4. Answer any one of the following:-

- 4-a. Using Thevenin's theorem, determine current and voltage in 2-Ω resistor in the circuit shown in Figure. (CO1) 10



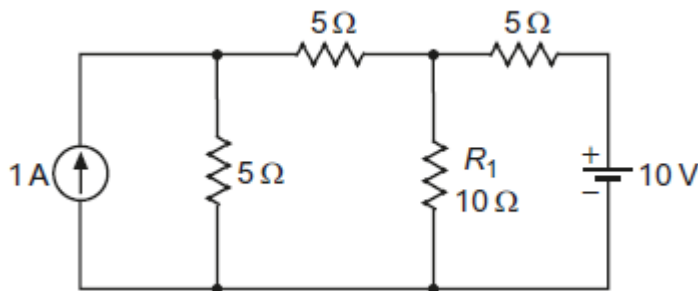- 4-b. Using mesh equation method, find current in the resistance R_1 of the network shown in Figure (CO1) 10



5. Answer any one of the following:-

- 5-a. A three phase voltage source has a line voltage of 400 V and supplies star connected load having impedance $(8 + j6) \Omega$ per phase, calculate line current, power factor and total three phase power supplied to the load. (CO2) 10
- 5-b. For an AC circuit expression of voltage and current are given as $v = 200 \sin(377t)$ V and $i = 8 \sin(377t - 30^\circ)$ A respectively. Find:(a)Power Factor (b) True Power (c)Apparent Power (d)Reactive Power (CO2) 10

6. Answer any one of the following:-

- 6-a. Explain why hysteresis and eddy current losses occur in transformer. How does change in efficiency affect the operation of given transformer?(CO3) 10
- 6-b. What is the importance of earthing? Discuss the difference between pipe earthing and rod earthing.(CO3) 10

7. Answer any one of the following:-

- 7-a. Difference between unregulated power supply and regulated power supply and How Zener diode act as a voltage regulator? (CO4) 10
- 7-b. Explain the Light Emitting Diodes (LED) with neat diagram. Write its Advantages and Disadvantages and its application in Brief. (CO4) 10

8. Answer any one of the following:-

- 8-a. Show that how input voltage gets reversed using operational amplifier. Also derive the expression for voltage gain using inverting amplifier.(CO5) 10
- 8-b. Explain the working of DMM with its block diagram. Also mention its advantages and disadvantages. (CO5) 10