Printed Page:- 03

Subject Code:- AEC0301

Roll. No:

NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA

(An Autonomous Institute Affiliated to AKTU, Lucknow)

B.Tech

SEM: III - THEORY EXAMINATION (2024- 2025) Subject: Digital System Design

Time: 3 Hours General Instructions:

IMP: Verify that you have received the question paper with the correct course, code, branch etc.
1. This Question paper comprises of three Sections -A, B, & C. It consists of Multiple Choice Questions (MCQ's) & Subjective type questions.
2. Maximum marks for each question are indicated on right -hand side of each question.
3. Illustrate your answers with neat sketches wherever necessary.
4. Assume suitable data if necessary.
5. Preferably, write the answers in sequential order.
6. No sheet should be left blank. Any written material after a blank sheet will not be

6. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.

SECTION-A

1. Attempt all parts:-

1-a. Which of following are known as universal gates? (CO1, K1)

- (a) NAND & NOR
- (b) AND & OR
- (c) NOR & OR
- (d) EX-NOR & XOR
- 1-b. The logic expression AB + A' B' can be implemented by giving inputs A and B to 1 a two-input (CO1,K6)
 - (a) NOR gate
 - (b) XNOR gate
 - (c) XOR gate
 - (d) NAND gate

1-c. A half adder circuit has two inputs and (CO2, K1)

- (a) one output
- (b) two output
- (c) three output
- (d) none of these
- 1-d. The output of SUM is equal to output of (CO2,K1)
 - (a) OR gate
 - (b) AND gate

Max. Marks: 100

20

1

1

1

	(c)	X-OR gate	
	(d)	X-Nor gate	
1-e.	Why latches are called memory devices? (CO3,K1)		
	(a)	It has capability to stare 8 bits of data	
	(b)	It has internal memory of 4 bit	
	(c)	It can store one bit of data	
	(d)	It can store infinite amount of data	
1-f.	W	hose operations are more faster among the following? (CO3,K1)	1
	(a)	Combinational circuits	
	(b)	Sequential circuits	
	(c)	Latches	
	(d)	Flip-flop	
1-g.	Т	he basic function of TTL gate is which of the following functions? (CO4,K1)	1
	(a)	AND	
	(b)	OR	
	(c)	NOR	
	(d)	NAND	
1-h.	С	MOS gates are commercially available as which of the following series? (CO4,	1
	K2)		
	(a)	1000	
	(b)	2000	
	(c)	3000	
	(d)	4000	
1-i.	A typical SRAM cell is made up ofTransistors. (CO5,K1)		1
	(a)	two	
	(b)	four	
	(c)	six	
	(d)	eight	
1-j.	F	or 5K memory, how many address lines are needed? (CO5,K6)	1
	(a)	10	
	(b)	13	
	(c)	12	
	(d)	9	
2. Att	empt	all parts:-	
2.a.	E	xplain the Demorgan's Theorem using example. (CO1,K1)	2
2.b.	D	efine Multiplexer. (CO2,K1)	2
2.c.	Write the truth table of T flip Flop.(CO3,K1)		
2.d.	L	ist out the advantages of CMOS logic family. (CO4,K1)	2

Page 2 of 3

•

2.e.	Compare EPROM to EEPROM. (CO5,K1)	2
SECTIC	<u>DN-B</u>	30
3. Answe	er any <u>five</u> of the following:-	
3-а.	Design basic gates using only NAND gates. (CO1,K6)	
3-b.	Explain Binary Codes.(CO1,K1)	6
3-с.	Explain 2 bit magnitude comparator with the help of diagram. (CO2,K1)	6
3-d.	Draw full adder using two half-adders and explain in detail (CO2,K2)	6
3.e.	Draw JK flip-flop and derive its characteristic equation. Explain how will you convert it into T flip-flop. (CO3,K1)	6
3.f.	List out the advantages and disadvantages of TTL logic families.(CO4,K1)	6
3.g.	Write a short note on PAL. (CO5,K1)	6
SECTIC	<u>DN-C</u>	50
4. Answe	er any <u>one</u> of the following:-	
4-a.	What is Hamming code? Construct the Hamming code for the data 1100 with (CO1,K6)	10
	a. even parity b. odd parity	
4-b.	Implement function $f(A,B,C,D) = \Sigma m(0,1,3,5,8,9,10)$ using 8:1 mux. (CO1,K6)	10
5. Answe	er any <u>one</u> of the following:-	
5-a.	Design 4-bit Binary to Gray code convertor. (CO2,K6)	10
5-b.	Explain encoder using proper diagram. (CO2,K1)	10
6. Answe	er any <u>one</u> of the following:-	
6-a.	What is counter? Design Mod-5 Synchronous counters. (CO3,K6)	10
6-b.	Differentiate between Ring and Johnson counter. (CO3,K1)	10
7. Answe	er any <u>one</u> of the following:-	
7-a.	Explain the following with respect to logic families: Fanout, Fan-In, Propagation delay and noise margin. (CO4,K1)	10
7-b.	Draw and explain working of TTL NAND gate and list out its prominent features. (CO4, K1)	10
8. Answe	er any <u>one</u> of the following:-	
8-a.	Draw the block diagram of PLA and explain the function of each block. (CO5,K1)	10
8-b.	Discuss in detail about internal structure of ROM and write types of ROM. (CO5,K2)	10

•