Printed Page:-04 Subject Code:- AEC0402 Roll. No: NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA (An Autonomous Institute Affiliated to AKTU, Lucknow) **B.** Tech SEM: IV - THEORY EXAMINATION (2024 - 2025) **Subject: Analog Circuit Time: 3 Hours** Max. Marks: 100 **General Instructions: IMP:** *Verify that you have received the question paper with the correct course, code, branch etc.* 1. This Question paper comprises of three Sections -A, B, & C. It consists of Multiple Choice *Questions (MCQ's) & Subjective type questions.* 2. Maximum marks for each question are indicated on right -hand side of each question. 3. Illustrate your answers with neat sketches wherever necessary. 4. Assume suitable data if necessary. 5. Preferably, write the answers in sequential order. 6. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked. **SECTION-A** 201. Attempt all parts:-1-a. During high frequency applications of a B.J.T, which parasitic capacitors arise 1 between the collector and the base?(CO1,K1) Cje and Cb (a) (b) Ccs (c) Сπ (d) Cμ 1-b. Current series feed back amplifier is also called as (CO1,K1) 1 **VCVS** (a) VCCS (b) CCCS (c) (d) CSVS/ 1 The common-mode gain is (CO2,K1) 1-c. (a) very high very low (b) always unity (c) unpredictable (d) 1-d. The input offset current equals the (CO2,K1) 1 difference between two base currents (a) (b) average of two base currents

	(c)	collector current divided by current gain	
	(d)	none of these	
1-e.	Ir	op-amp differentiator circuit the capacitor is(CO3,K1)	1
	(a)	Feedback element	
	(b)	Input element	
	(c)	Both of these	
	(d)	None of these	
1-f.	А	third order filter will have a roll off rate of(CO3,K1)	1
	(a)	-20dB/decade	
	(b)	-30 dB /decade	
	(c)	-60 dB /decade	
	(d)	-40 dB/decade	
1-g.	W ((Which among the following does not belong to the category of LC oscillators? CO4,K1)	1
	(a)	Hartley oscillator	
	(b)	Colpitts oscillator	
	(c)	Clapp oscillator	
	(d)	Wein bridge oscillator	
1-h.	С	lapp oscillator is an improved version of (CO4,K1)	1
	(a)	LC oscillator	
	(b)	RC oscillator	
	(c)	RL oscillator	
	(d)	Relaxation oscillator	
1-i.	Т	he current source which has a very high output resistance? (CO5,K1)	1
	(a)	Simple current mirror	
	(b)	Wilson current mirror	
	(c)	Widlar current mirror	
	(d)	All of the mentioned	
1-j.	How to improve CMRR value? (CO5,K1)		
	(a)	Increase common mode gain	
	(b)	Decrease common mode gain	
	(c)	Decrease Differential mode gain	
	(d)	None of the above	
2. Att	empt a	all parts:-	
2.a.	W	hat do you understand of frequency response of an amplifier? (CO1,K2)	2
2.b.	D	raw the transfer characteristic and equivalent circuit of an Op-Amp. (CO2,K2)	2
2.c.	W	That are the advantages of active filters over Passive filters? (CO3,K2)	2
2.d.	D	iscuss the Barkhausen criterion for sustained oscillations. (CO4,K2)	2

Page 2 of 4

•

2.e.	What do you understand by compliance voltage in case of current mirror? (CO5,K2)	2		
SECTIO	<u>SECTION-B</u>			
3. Answe	er any <u>five</u> of the following:-			
3-a.	Explain the operation of class B Power amplifier with necessary waveforms. (CO1,K2)	6		
3-b.	Show that the lower cutoff frequency of multistage amplifier is higher than the lower cutoff frequency of single stage amplifier. (CO1,K2)	6		
3-с.	Define the AC and DC parameters of Op-amp. (CO2,K2)	6		
3-d.	Compare ideal and practical parameters of Op-amp. (CO2,K2)	6		
3.e.	Derive the expression for output voltage of an integrator circuit and also write its applications. (CO3,K3)	6		
3.f.	Explain the Operation of Wien Bridge Oscillator with neat diagram and give the condition for sustained oscillation. (CO4,K3)	6		
3.g.	An op-amp with a differential gain of $A_d = 4000$ is supplied with input voltages of Vi ₁ =150 µV and Vi ₂ =140 µV. Determine the output voltage if the value of CMRR is 1000. (CO5,K2)	6		
SECTIO	SECTION-C			
4. Answer any <u>one</u> of the following:-				
4-a.	Explain the voltage series feedback amplifier and also calculate amplifier gain, input impedance, and output impedance. (CO1,K3)	10		
4-b.	Derive the expression for higher cutoff frequency of single stage CS/CE amplifier. (CO1,K3)	10		
5. Answe	er any <u>one</u> of the following:-			
5-a.	Discuss an Op-Amp based voltage follower circuit with advantages. (CO2,K3)	10		
5-b.	What is an Op-amp? Determine the output voltage for the circuit of fig. V1 = 5 Volt and V ₂ = 10 Volt. (CO2,K3)	10		
	\mathbf{C}			

•



- 6. Answer any one of the following:-
- 6-a. Discuss with neat diagram the Schmitt trigger ith waveform and write its 10 applications. (CO3,K3)
- 6-b. Draw and explain the block diagram of IC 555 Timer. Also, write the expression 10 of output frequency for astable multivibrator. (CO3,K3)
- 7. Answer any one of the following:-
- 7-a. Draw the circuit diagram of RC phase shift Oscillator and Explain its working. 10 (CO4,K3)
- 7-b. Draw Hartley Oscillator Circuit. In a Hartley oscillator, the value of the capacitor 10 in the tuned circuit is 500 p F and the two sections of coil have inductances 38μ H and 12μ H. Find the frequency of oscillations and the feedback factor β . (CO4,K3)
- 8. Answer any one of the following:-
- 8-a. Draw and explain the Wilson BJT current mirror. Also discuss in detail how it 10 can be improved. (CO5,K3)
- 8-b. Draw and derive the expression of current transfer ratio of modified current 10 mirror. (CO5,K3)