

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA

(An Autonomous Institute Affiliated to AKTU, Lucknow)

B.Tech

SEM: III - THEORY EXAMINATION (2024 - 2025)

Subject: Logic Design and Microcontroller

Time: 3 Hours

Max. Marks: 100

General Instructions:*IMP: Verify that you have received the question paper with the correct course, code, branch etc.**1. This Question paper comprises of three Sections -A, B, & C. It consists of Multiple Choice Questions (MCQ's) & Subjective type questions.**2. Maximum marks for each question are indicated on right -hand side of each question.**3. Illustrate your answers with neat sketches wherever necessary.**4. Assume suitable data if necessary.**5. Preferably, write the answers in sequential order.**6. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.***SECTION-A**

20

1. Attempt all parts:-

1-a. The Octal equivalent of Binary number 1101 is----. (CO1,K1)

1

- (a) 11
- (b) 12
- (c) 13
- (d) 15

1-b. Which of the following circuit can be used as parallel to serial converter? (CO1,K1)

1

- (a) Multiplexer
- (b) Demultiplexer
- (c) Decoder
- (d) Digital counter

1-c. In the Moore circuit/ machine, the output depends _____. (CO2,K1)

1

- (a) Only on inputs
- (b) Only on states
- (c) Both on input and states
- (d) None of these

1-d. The race around condition is related to-----flip-flop. (CO2,K1)

1

- (a) S R
- (b) T

- (c) J K
- (d) D
- 1-e. What is stored in the H & L general-purpose register? (CO3,K1) 1
- (a) Opcode
- (b) Address of memory
- (c) Address of next instruction
- (d) Temporary data
- 1-f. What is the function of STC instruction? (CO3,K1) 1
- (a) Store to C Register, the value of Accumulator
- (b) Set Carry to 1
- (c) Clear the Stack pointer
- (d) Set SP to 1
- 1-g. What does the term "pin-muxing" refer to in the context of GPIO? (CO4,K1) 1
- (a) Configuring a pin for multiple functions
- (b) Combining multiple pins into one
- (c) Using multiple pins for a single function
- (d) Disabling unused pins
- 1-h. The AVR CPU core operates based on which architecture? (CO4,K1) 1
- (a) RISC
- (b) CISC
- (c) VLIW
- (d) Multithreading
- 1-i. Which PWM mode has a symmetric waveform, counting up and then down? (CO5,K1) 1
- (a) Fast PWM
- (b) Normal mode
- (c) Phase Correct PWM
- (d) CTC mode
- 1-j. What is the primary function of an Analog Comparator in ATmega328P? (CO5,K1) 1
- (a) Compare two analog voltages
- (b) Generate a digital signal
- (c) Control the clock source
- (d) Generate PWM signals
2. Attempt all parts:-
- 2.a. Define the base (radix) of a number system. Convert $(35.25)_{10}$ into binary number. (CO1,K2) 2
- 2.b. Give the comparison between combinational circuits and sequential circuits. 2

(CO2,K2)

- 2.c. List the 16 – bit registers of 8085 microprocessor. (CO3,K1) 2
- 2.d. Explain the role of the SRAM in ATmega 328P. (CO4,K2) 2
- 2.e. Define the purpose of Timer/Counters in ATmega328P. (CO5,K2) 2

SECTION-B

30

3. Answer any five of the following:-

- 3-a. Design a 2- bit magnitude comparator using gates. (CO1,K3) 6
- 3-b. What is Demultiplexer? Design 1 :16 demux using 1:4 demux. (CO1,K3) 6
- 3-c. Explain 4 bit Johnson counter with circuit diagram and waveforms. (CO2,K3) 6
- 3-d. Convert T flip-flop into D flip-flop. (CO2,K3) 6
- 3.e. Explain following signals of 8085. a) ALE b) READY c) INTR (CO3,K2) 6
- 3.f. Draw the architecture of the AVR CPU core of the atmega328P microcontroller. (CO4,K2) 6
- 3.g. Describe how fast PWM mode differs from phase-correct PWM mode. (CO5,K3) 6

SECTION-C

50

4. Answer any one of the following:-

- 4-a. Simplify the given function using K-map technique in SOP and POS forms: (CO1,K3) 10

$$F(w,x,y,z) = \sum m(0,1,7,8,9,10,12) + \sum d(2,5,15).$$

- 4-b. Design and explain carry look ahead adder. (CO1,K3) 10

5. Answer any one of the following:-

- 5-a. Draw & explain working of universal shift register. (CO2,K3) 10
- 5-b. Convert D and JK flip-flopes into T flip-flop. (CO2,K3) 10

6. Answer any one of the following:-

- 6-a. With the help of neat diagram explain the architecture of 8085 microprocessor in detail. Discuss its flag register. (CO3,K3) 10
- 6-b. Specify the contents of the A,B,C,D,E,H,L ,M registers as each if the following instructions is being executed. MVI C,FFH LXI H,2030H LXI D,7050H MOV M,C XCHG LDAX D HLT (CO3,K3) 10

7. Answer any one of the following:-

- 7-a. Draw the schematics of the PIN muxing and Internal Pull up resistor and discuss their requirements in brief. (CO4,K3) 10
- 7-b. Draw the block diagram of the ATmega328P microcontroller and explain each component in detail. (CO4,K3) 10

8. Answer any one of the following:-

- 8-a. Discuss about the ASSR and GTCCR register in detail. (CO5,K3) 10
- 8-b. Describe the working of SPI and IIC protocol? How they are used in atmega328P and how they differ from USART. (CO5,K3) 10