

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA

(An Autonomous Institute Affiliated to AKTU, Lucknow)

B.Tech

SEM: III - THEORY EXAMINATION (2024 - 2025)

Subject: Analog Circuits

Time: 3 Hours

Max. Marks: 100

General Instructions:

IMP: Verify that you have received the question paper with the correct course, code, branch etc.

1. This Question paper comprises of three Sections -A, B, &amp; C. It consists of Multiple Choice Questions (MCQ's) &amp; Subjective type questions.

2. Maximum marks for each question are indicated on right -hand side of each question.

3. Illustrate your answers with neat sketches wherever necessary.

4. Assume suitable data if necessary.

5. Preferably, write the answers in sequential order.

6. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.

**SECTION-A**

20

1. Attempt all parts:-

1-a. How many terminals can a MOSFET have? (CO1, K1)

1

- (a) 2
- (b) 5
- (c) 1
- (d) 3 or 4

1-b. The upper cutoff frequency of multistage amplifier is .....than the upper cutoff frequency of single stage amplifier. (CO1,K1)

1

- (a) equal or more
- (b) more
- (c) less
- (d) None of the above

1-c. In the power amplifier the efficiency .....from class A to class C mode. (CO2,K1)

1

- (a) increases
- (b) decreases
- (c) constant
- (d) None of these

1-d. Which of the following class have a theoretical efficiency of 78.5%? (CO2, K1)

1

- (a) Class A

- (b) Class D  
(c) Class C  
(d) Class B
- 1-e. An noninverting amplifier has voltage gain of 10. Find the output voltage for  $V_{in} = 5V$ . (CO3,K2) 1
- (a) 50V  
(b) -50V  
(c)  $+V_{sat}$   
(d)  $-V_{sat}$
- 1-f. A certain OP-amp has bias currents of  $50 \mu A$  and  $49 \mu A$ . The input bias current is .... (CO3, K2) 1
- (a)  $1 \mu A$   
(b)  $99.3 \mu A$   
(c)  $49.5 \mu A$   
(d) None of the mentioned
- 1-g. A differential amplifier is capable of amplifying (CO4, K1) 1
- (a) DC input signal only  
(b) AC input signal only  
(c) AC & DC input signal both  
(d) None of the Mentioned
- 1-h. The compliance voltage is related to.....(CO4, K2) 1
- (a) oscillators  
(b) current mirrors  
(c) amplifiers  
(d) Power amplifiers
- 1-i. Which of the following is not an example of non-sinusoidal oscillator? (CO5, K1) 1
- (a) Sawtooth Generators  
(b) UJT relaxation oscillator  
(c) Multivibrator  
(d) Colpitts oscillator
- 1-j. Clap oscillator is the improved version of..... (CO5, K1) 1
- (a) Phase shift oscillator  
(b) Colpitts Oscillator  
(c) Wein bridge Oscillator  
(d) Crystal Oscillator

2. Attempt all parts:-

- 2.a. Write the difference between of FET and BJT. (CO1, K1) 2
- 2.b. Define the terms Efficiency, Power dissipation and Distortion of power 2

amplifier. (CO2, K1)

- 2.c. Draw and explain unity gain amplifier. (CO3, K2) 2
- 2.d. What are the characteristics of current mirror? (CO4, K1) 2
- 2.e. Write the Barkhausen Criterion for sustained oscillations. (CO5, K1) 2

### **SECTION-B**

30

3. Answer any five of the following:-

- 3-a. Draw and explain the Frequency response of single and multistage amplifiers. (CO1, K1, K2) 6
- 3-b. Draw the small signal model for CS amplifier and calculate its different parameters. (CO1, K1, K2) 6
- 3-c. Compare the different feedback topologies with respect to input and output resistances. (CO2, K1) 6
- 3-d. Explain the operation of class A Power amplifier with necessary waveforms. (CO2, K1) 6
- 3.e. Draw and explain the Schmitt Trigger Circuit with hysteresis curve. (CO3, K1, K2) 6
- 3.f. What is a current mirror? For modified current mirror, show that  $I_{out} = I_{ref} / [1 + 2/\beta(1 + \beta)]$ . (CO4, K1, K2) 6
- 3.g. Explain the Operation of RC phase shift Oscillator with neat diagram and give the condition for sustained oscillation. (CO5, K1, K2) 6

### **SECTION-C**

50

4. Answer any one of the following:-

- 4-a. Draw the high and low frequency transistor model of CE amplifier and derive the expression for cutoff frequencies with its frequency response. (CO1, K1, K2) 10
- 4-b. Explain small signal equivalent model for CE amplifier. Calculate Input Resistance  $R_i$ , Output Resistance  $R_o$ , and Voltage gain  $A_v$ . (CO1, K1, K2) 10

5. Answer any one of the following:-

- 5-a. Draw the circuit of class B amplifier. Explain the crossover distortion in class B amplifier and explain how it can be reduced? (CO2, K1, K2) 10
- 5-b. Explain the current series feedback amplifier and also calculate amplifier gain, input impedance, and output impedance. (CO2, K1, K2) 10

6. Answer any one of the following:-

- 6-a. Draw and explain super diode in precision half wave rectifier circuit. Also, write its advantages and applications. (CO3, K1, K2) 10
- 6-b. Design a second order band pass Butterworth filter with lower and higher cutoff frequency of 500Hz & 1500Hz respectively. Draw the designed circuit and frequency response for the pass band gain of 4. (CO3, K1, K2) 10

7. Answer any one of the following:-

- 7-a. Draw and derive the expression of current transfer ratio of improved Wilson 10

current mirror. (CO4,K1,K2)

- 7-b. Draw the circuit of simple current mirror. Derive current transfer ratio for simple current mirror. Also discuss the advantages and disadvantages of current mirror circuits with their applications. (CO4, K2) 10

8. Answer any one of the following:-

- 8-a. Explain the working of Wein Bridge Oscillator with the help of circuit diagram. Write the expression for frequency of oscillation. A wein bridge oscillator has a frequency of 500 kHz, if the value of C is 1000pF, determine the value of R. (CO5, K1, K2) 10
- 8-b. Explain the working of Astable multivibrator using IC555 with its circuit diagram and waveform. (CO5, K1, K2) 10

COP:JULY\_DEC-2024