

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA

(An Autonomous Institute Affiliated to AKTU, Lucknow)

MCA (Integrated)

SEM: I - THEORY EXAMINATION (2024 - 2025)

Subject: Digital Logic & Circuit Design

Time: 3 Hours

Max. Marks: 100

General Instructions:*IMP: Verify that you have received the question paper with the correct course, code, branch etc.**1. This Question paper comprises of three Sections -A, B, & C. It consists of Multiple Choice Questions (MCQ's) & Subjective type questions.**2. Maximum marks for each question are indicated on right -hand side of each question.**3. Illustrate your answers with neat sketches wherever necessary.**4. Assume suitable data if necessary.**5. Preferably, write the answers in sequential order.**6. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.***SECTION-A**

20

1. Attempt all parts:-

1-a. $A+B=B+A$ is called as ----- . (CO1,K1)

1

- (a) Associative law
- (b) Commutative law
- (c) Idempotent law
- (d) None

1-b. Gray code of binary number 0101 is: (CO1,K1)

1

- (a) 0010
- (b) 0001
- (c) 0111
- (d) 0110

1-c. A combinational circuit that takes only 1 input and gives multiple output is--- (CO2,K1)

1

- (a) MUX
- (b) DEMUX
- (c) Decoder
- (d) Encoder

1-d. A code converter is a logic circuit that _____ (CO2,K1)

1

- (a) Inverts the given input
- (b) Converts into decimal number

- (c) Converts data of one type into another type
- (d) Converts to octal
- 1-e. Latch is the basic building block of: (CO3,K1) 1
- (a) Flip flop
- (b) Buffer
- (c) Gate
- (d) None
- 1-f. The arithmetic operation that can be performed by doing a Left shift is: (CO3,K1) 1
- (a) Addition
- (b) Subtraction
- (c) Multiplication
- (d) Division
- 1-g. The diagram that shows the transition of states is known as: (CO4,K1) 1
- (a) Transition diagram
- (b) State Table
- (c) Both of above
- (d) None
- 1-h. A type of FSM where the outputs depend only on the current state. (CO4,K1) 1
- (a) Deterministic FSM
- (b) Mealy machine
- (c) Moore machine
- (d) Non- Deterministic
- 1-i. The fundamental building blocks of IoT networks are: (CO5,K1) 1
- (a) Sensors
- (b) Object
- (c) Physical thing
- (d) Sensor network
- 1-j. GPS stands for: (CO5,K1) 1
- (a) Global positioning system
- (b) Global parity system
- (c) Geo positioning system
- (d) Global position software

2. Attempt all parts:-

- 2.a. Find the decimal equivalent of $(101101.1)_2$ (CO1,K2) 2
- 2.b. Draw the circuit diagram of 1-bit magnitude comparator. (CO2,K1) 2
- 2.c. How many types of shift registers are there and write their names also? (CO3,K1) 2
- 2.d. Write the significance of State Table. (CO4,K2) 2

2.e.	Write some advantages of IoT. (CO5,K2)	2
SECTION-B		30
3.	Answer any <u>five</u> of the following:-	
3-a.	Perform A-B using 1's and 2's complements for A= 1100 and B= 0111. (CO1,K2)	6
3-b.	Discuss with truth table NAND, NOR &, EXOR gates. (CO1,K2)	6
3-c.	Design a full Adder using two half adders. (CO2,K2)	6
3-d.	Design a 3-bit Binary to Gray code convertor. (CO2,K3)	6
3.e.	Discuss Ring counter and its working. (CO3,K2)	6
3.f.	Compare Mealy and Moore Machines in detail. (CO4,K2)	6
3.g.	Discuss the following: a) Temperature sensor b) Proximity sensor and c) IR sensor (CO5,K2)	6
SECTION-C		50
4.	Answer any <u>one</u> of the following:-	
4-a.	Simplify the function $F(A,B,C,D) = \sum(0,,2,5,7,8,10,13,15) + d(6,14)$ in SOP form and implement using logic gates. (CO1,K3)	10
4-b.	Explain the following terms with suitable example: a) Maxterm and b) Minterm (CO1,K3)	10
5.	Answer any <u>one</u> of the following:-	
5-a.	Implement $F(A, B, C, D) = \sum(0,1,3,4,8,9,11,15)$ using 8x1 multiplexer: If MSB i.e. A is used as input variable and B, C, D as select lines. (CO2,K3)	10
5-b.	Implement full subtractor using Decoder. (CO2,K3)	10
6.	Answer any <u>one</u> of the following:-	
6-a.	Realize T flip flop using D flip flop. (CO3,K3)	10
6-b.	Design MOD-5 synchronous counter. (CO3,K3)	10
7.	Answer any <u>one</u> of the following:-	
7-a.	Explain static and dynamic hazard with proper examples. (CO4,K3)	10
7-b.	Explain propagational delay and its role in hazard occurrence. (CO4,K3)	10
8.	Answer any <u>one</u> of the following:-	
8-a.	Discuss the core components of Machine-to- machine (M2M) architecture and explain their roles in enabling seamless communication between devices. (CO5,K3)	10
8-b.	With circuit diagram, explain the working of Node MCU board. (CO5,K3)	10