

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA
(An Autonomous Institute Affiliated to AKTU, Lucknow)

B.Tech

SEM: I - THEORY EXAMINATION (2025 - 2026)

Subject: Digital Electronics and IoT Systems

Time: 3 Hours

Max. Marks: 100

General Instructions:

IMP: Verify that you have received the question paper with the correct course, code, branch etc.

1. This Question paper comprises of **three Sections -A, B, & C**. It consists of Multiple Choice Questions (MCQ's) & Subjective type questions.

2. Maximum marks for each question are indicated on right -hand side of each question.

3. Illustrate your answers with neat sketches wherever necessary.

4. Assume suitable data if necessary.

5. Preferably, write the answers in sequential order.

6. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.

SECTION-A

20

1. Attempt all parts:-

- 1-a. What is the binary equivalent of $(25)_{10}$?(CO1 K1) 1
- (a) 11001
- (b) 11101
- (c) 10101
- (d) 10011
- 1-b. What is the result of $1101 + 1010$ in binary?(CO1 K1) 1
- (a) 11111
- (b) 10111
- (c) 11001
- (d) 10001
- 1-c. The output of full adder SUM is equal to (CO2,K1) 1
- (a) $X \cdot Y \cdot Z$
- (b) $X + Y + Z$
- (c) $X + Y \cdot Z$
- (d) $X \oplus Y \oplus Z$
- 1-d. One that is not the outcome of magnitude comparator is ____ (CO2,K2) 1
- (a) $a < b$
- (b) $a - b$
- (c) $a > b$
- (d) $a = b$
- 1-e. SR latch made using NAND gates becomes active when inputs are:(CO3 K1) 1

- (a) HIGH
 (b) LOW
 (c) Floating
 (d) Pulsed
- 1-f. A Master-Slave flip-flop is used to: (CO3 K1) 1
 (a) Amplify signal
 (b) Avoid race condition
 (c) Convert analog to digital
 (d) Reduce noise
- 1-g. To provide parallel output, clock pulse are used in SIPO Register are _____.(CO4,K1) 1
 (a) n+2
 (b) n-2
 (c) n
 (d) 0
- 1-h. A 4-bit counter has a maximum modulus of _____.(CO4,K1) 1
 (a) 3
 (b) 6
 (c) 8
 (d) 16
- 1-i. LDR sensor is used to measure:(CO5,K2) 1
 (a) Light intensity
 (b) Temperature
 (c) Humidity
 (d) Sound
- 1-j. What is the voltage level of HIGH in Arduino UNO?(CO5,K2) 1
 (a) 0V
 (b) 2.5V
 (c) 3.3V
 (d) 5V

2. Attempt all parts:-

- 2.a. What is a universal gate? Give examples.(CO1,K1) 2
 2.b. $F(A,B,C) = \sum m(1,4,5,7)$ minimize the given using K-MAP in SOP form. (CO2,K3) 2
 2.c. With reference to a J-K flip-flop, what is racing? (CO3 K1) 2
 2.d. Draw the timing diagram of '1010' in SIPO register.(CO4,K1) 2
 2.e. Mention any two key characteristics of IoT.(CO5,K2) 2

SECTION-B 30

3. Attempt all parts:-

3.a. Answer any one of the following:-

- 3.a.(i) Convert the following: (i) $4FA_{16} \rightarrow$ Binary and Decimal (ii) $1011.101_2 \rightarrow$ 6

Decimal and Octal(CO1 K2)

- 3.a.(ii) Implement NOT, OR, AND & NOR Gates using NAND Gate only. (CO1 K2) 6
- 3.b. Answer any one of the following:-
- 3.b.(i) Explain full subtractor with proper logic circuit diagram. Implement it using half subtractor. (CO2,K2) 6
- 3.b.(ii) Design a 16:1 MUX using 2:1 MUX. (CO2,K3) 6
- 3.c. Answer any one of the following:-
- 3.c.(i) Define race around condition with suitable diagram, how to remove it. (CO3 K2) 6
- 3.c.(ii) Convert SR flip-flop to JK flip-flop. Provide truth table, conversion steps, and logic diagram. (CO3 K1) 6
- 3.d. Answer any one of the following:-
- 3.d.(i) Show the timing diagram of '1111' in : a)Serial-in serial-out shift register b) Parallel-in serial-out shift register .(CO4,K2) 6
- 3.d.(ii) Design a MOD-8 Asynchronous UP counter using T flip-flops. Draw its timing diagram.(CO4,K2) 6
- 3.e. Answer any one of the following:-
- 3.e.(i) Discuss various real-world applications of IoT in healthcare, agriculture, and smart cities.(CO5,K2) 6
- 3.e.(ii) What are sensors and actuators? Explain their working and types used in IoT with examples.(CO5,K2) 6

SECTION-C

50

4. Answer any one of the following:-

- 4-a. (i)What is hamming code; encode a binary word 1111 into the even parity hamming code.(CO1 K2) 10
(ii)What are universal gates.Implement OR,AND NOR using NAND gate. (CO1 K2)
- 4-b. (i) Convert the following:(CO1 K2) 10
(a) $(3656)_{10} = ()_{BCD}$
(b) $(1110)_2 = ()_{GREY}$
(c) $(1001)_2 = ()_{EXCESS\ 3}$
(d) $(10100001011)_2 = ()_8$
(e) $(1110111101101)_2 = ()_{16}$
(ii) Simplify the following $Y = ((AB)' + A' + AB)'$

5. Answer any one of the following:-

- 5-a. Explain and design BCD to gray code conversion circuit.(CO2,K3) 10
- 5-b. Simplify the logic function $F(A, B, C, D) = \sum (1,4,8,12,13,15) + d(3,14)$ using K-map in SOP form and draw the logic circuit. Also minimize it using POS. (CO2,K3) 10


6. Answer any one of the following:-

- 6-a. Discuss the working of J-K flip-flop with truth table, characteristic equation, and excitation table.(CO3 K2) 10
- 6-b. Design a 3 bit Synchronous DOWN counter and draw its logic circuit using T flip 10

flop. (CO3 K2)

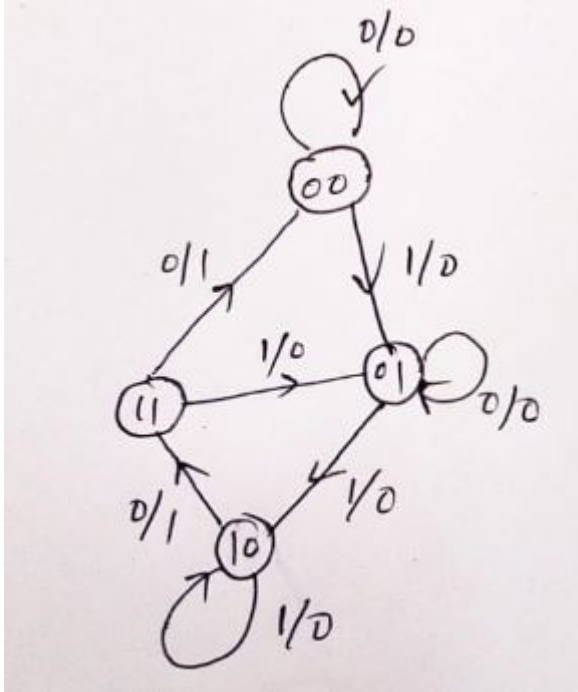7. Answer any one of the following:-

- 7-a. (i) Differentiate between RAM and ROM? (CO4,K3) 10
(ii) Draw circuit and state diagram for '1011' in Ring counter?(CO4,K3)
- 7-b. Design a synchronous sequential circuit using T flip flop Of the given state diagram showing state table (CO4,K3) 10



8. Answer any one of the following:-

- 8-a. Explain in detail the key characteristics of IoT: Interconnectivity, Heterogeneity, Scalability, Intelligence, and Security. Also discuss its key components?(CO5,K2) 10
- 8-b. Explain the 5-layer architecture of IoT: Perception, Network, Middleware, Application, and Business layers. Use a diagram.(CO5,K2) 10