

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA
(An Autonomous Institute Affiliated to AKTU, Lucknow)

B.Tech

SEM: III - THEORY EXAMINATION (2025- 2026)

Subject: Digital System Design

Time: 2 Hours

Max. Marks: 50

General Instructions:

IMP: Verify that you have received the question paper with the correct course, code, branch etc.

1. This Question paper comprises of **three Sections -A, B, & C**. It consists of Multiple Choice Questions (MCQ's) & Subjective type questions.

2. Maximum marks for each question are indicated on right -hand side of each question.

3. Illustrate your answers with neat sketches wherever necessary.

4. Assume suitable data if necessary.

5. Preferably, write the answers in sequential order.

6. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.

SECTION-A

15

1. Attempt all parts:-

- 1-a. In four-variable K-map simplification, a group of eight adjacent ones leads to a term with (CO1,K3) 1
- (a) one literal
- (b) two literal
- (c) three literal
- (d) four literal
- 1-b. A code converter is a logic circuit that _____ (CO2,K2) 1
- (a) Inverts the given input
- (b) Converts into decimal number
- (c) Converts data of one type into another type
- (d) Converts to octal
- 1-c. _____ are the applications of flip flop. (CO3,K4) 1
- (a) registers
- (b) counter
- (c) storage devices
- (d) all of the above
- 1-d. How many flip-flops are required to construct a decade counter? (CO4,K3) 1
- (a) 4
- (b) 8
- (c) 5
- (d) 10

- 1-e. FPGA stands for: (CO5,K1) 1
- (a) Complex Programmable Logic Device
 - (b) Configurable Programmable Logic Device
 - (c) Field Programmable Gate Array
 - (d) Combined Programmable Logic Device

2. Attempt all parts:-

- 2.a. Implement $Y = AB + CD$ using NAND gate only. (CO1, K3) 2
- 2.b. Define encoder. (CO2,K2) 2
- 2.c. Using the characteristic table of an D flip-flop, construct the K-map and derive its characteristic equation.(CO3,K4) 2
- 2.d. What do you mean by sequential circuit? (CO4,K1) 2
- 2.e. Differentiate between volatile and non-volatile memory. (CO5,K2) 2

SECTION-B

15

3. Attempt all parts:-

3.a. Answer any one of the following:-

- 3.a.(i) Minimize the function $F(W, X, Y, Z) = m(1, 2, 6, 7, 8, 13, 14, 15) + d(0, 3, 5, 12)$ using K-Map (CO1,K4) 3

- 3.a.(ii) Minimize the function $F(A,B,C,D,E) = \sum m(0,2,4,7,8,10,12,16,18,20,23,24,25,26,27,28)$ using K-Map. (CO1,K4) 3

3.b. Answer any one of the following:-

- 3.b.(i) Design a full adder using two half adders and OR gate. Also write an expression for sum and carry output. (CO2, K3) 3

- 3.b.(ii) Design a combinational circuit that accepts a three-bit number and generates an output binary number equal to the square of the input number. (CO2,K5) 3

3.c. Answer any one of the following:-

- 3.c.(i) Explain Johnson counter in detail with the help of circuit diagram. Write its another popular name. (CO3,K2) 3

- 3.c.(ii) Explain the race-around condition in JK flip-flop and write the three ways it can be avoided. (CO3,K2) 3

3.d. Answer any one of the following:-

- 3.d.(i) Design a MOD-5 synchronous UP Counter. (CO4, K4) 3

- 3.d.(ii) Design 3-bit ripple UP Counter. Draw its state diagram, state table and logic diagram. (CO4, K4) 3

3.e. Answer any one of the following:-

- 3.e.(i) Implement the following Boolean functions using PROM. (CO5,K4) 3

$$F1(A, B, C) = \sum m(5,6,7),$$

$$F2(A, B, C) = \sum m(3,5,6,7)$$

- 3.e.(ii) Implement the sum and carry expressions of full adder expressions using PLA and PAL. (CO5,K5) 3

SECTION-C

20

4. Answer any one of the following:-
- 4-a. Perform the subtraction $(110010_2) - (010101_2)$ using the 1's and 2's complement method. (CO1,K3) 4
- 4-b. A Hamming (12,8) received codeword is: **110101101001**. Find the error position and correct it. Use even parity (CO1,K3) 4
5. Answer any one of the following:-
- 5-a. Design an **8-to-3 priority encoder** and explain how priority is handled. (CO2, K3) 4
- 5-b. Design a 2 bit magnitude comparator. (CO2, K3) 4
6. Answer any one of the following:-
- 6-a. Explain the working of a Universal Shift Register with the help of block diagram. (CO3,K2) 4
- 6-b. Convert T flip-flop into D flip-flop. (CO3,K3) 4
7. Answer any one of the following:-
- 7-a. Design 101 sequence detector using Mealy Machines. (CO4, K5) 4
- 7-b. Explain the types of hazards and how redundant term help in reducing the hazards in circuits. (CO4, K3) 4
8. Answer any one of the following:-
- 8-a. Differentiate between FPGA and CPLD. (CO5, K2) . 4
- 8-b. Explain the working of ROM, PROM, EPROM, and EEPROM. (CO5, K2) 4