

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA

(An Autonomous Institute Affiliated to AKTU, Lucknow)

B.Tech

SEM: III - THEORY EXAMINATION (2023 - 2024)

Subject: Logic Design and Microcontroller

Time: 3 Hours

Max. Marks: 100

General Instructions:

IMP: Verify that you have received the question paper with the correct course, code, branch etc.

1. This Question paper comprises of **three Sections -A, B, & C**. It consists of Multiple Choice Questions (MCQ's) & Subjective type questions.
2. Maximum marks for each question are indicated on right -hand side of each question.
3. Illustrate your answers with neat sketches wherever necessary.
4. Assume suitable data if necessary.
5. Preferably, write the answers in sequential order.
6. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.

SECTION-A

20

1. Attempt all parts:-

- 1-a. There are _____ cells in a 4-variable K-map. (CO1) 1
- (a) 12
 - (b) 16
 - (c) 18
 - (d) 8
- 1-b. What is a multiplexer? (CO1) 1
- (a) It is a type of decoder which decodes several inputs and gives one output
 - (b) A multiplexer is a device which converts many signals into one
 - (c) It takes one input and results into many output
 - (d) It is a type of encoder which decodes several inputs and gives one output
- 1-c. A basic S-R flip-flop can be constructed by cross-coupling of which basic logic gates? (CO2) 1
- (a) AND or OR gates
 - (b) XOR or XNOR gates
 - (c) NOR or NAND gates
 - (d) AND or NOR gates
- 1-d. What is the difference between a shift-right register and a shift-left register? (CO2) 1
- (a) There is no difference

- (b) The direction of the shift
- (c) Propagation delay
- (d) The clock input
- 1-e. Which of the following is not correct about HLT instruction? (CO3) 1
- (a) It is a machine control instruction
- (b) It is used to start the execution of the program
- (c) PC is disconnected from the address bus
- (d) A reset interrupt is required to come out of halt state
- 1-f. Which of the following flag is used to mask INTR interrupt? (CO3) 1
- (a) zero flag
- (b) auxiliary carry flag flag
- (c) interrupt flag
- (d) sign flag
- 1-g. After RETI instruction is executed then the pointer will move to which location in the program? (CO4) 1
- (a) Next interrupt of the interrupt vector table
- (b) Immediate next instruction where interrupt is occurred
- (c) Next instruction after the RETI in the memory
- (d) None of the mentioned
- 1-h. Which of the following registers are not bit addressable? (CO4) 1
- (a) SCON
- (b) PCON
- (c) A
- (d) PSW
- 1-i. Vector address for Timer 1 Interrupt is (CO5) 1
- (a) 0003H
- (b) 000BH
- (c) 0013H
- (d) 001BH
- 1-j. EA bit is used to_____. (CO5) 1
- (a) enable or disable external interrupts
- (b) enable or disable internal interrupts
- (c) enable or disable all the interrupts
- (d) none of the mentioned
2. Attempt all parts:-
- 2.a. What are the universal logic gates? (CO1) 2
- 2.b. State the difference between Synchronous and Asynchronous counters. (CO2) 2
- 2.c. What are the various registers in 8085? (CO3) 2

- 2.d. Write a short note on Immediate addressing mode. (CO4) 2
- 2.e. Explain different types of memory. (CO5) 2

SECTION-B

30

3. Answer any five of the following:-

- 3-a. Simplify: $f(A,B,C,D) = \sum m(1,3,5,7,8,9,11,13,15)$ using POS form. (CO1) 6
- 3-b. Design 1:16 demux using 1:4 demux. (CO1) 6
- 3-c. Draw and explain the operation of T Flip-Flop. (CO2) 6
- 3-d. What is ring counter? Explain 4-bit ring counter. (CO2) 6
- 3.e. What is bus? Explain different types of buses. (CO3) 6
- 3.f. Write a program to perform 8-bit addition and 8-bit subtraction in 8051. (CO4) 6
- 3.g. Write down the programming steps for serial data transmission. (CO5) 6

SECTION-C

50

4. Answer any one of the following:-

- 4-a. $F(A,B,C,D,E) = \sum m(4,5,7,8,10,14,27,31) + \sum d(0,1,2,11,19,25)$ minimize the given using K-MAP in SOP form. (CO1) 10
- 4-b. Design a 4-bit parallel adder using gates. (CO1) 10

5. Answer any one of the following:-

- 5-a. Design a MOD4 down counter using T flip flop. (CO2) 10
- 5-b. Realize SR flip flop using NOR gates and explain its operation. (CO2) 10

6. Answer any one of the following:-

- 6-a. Explain arithmetic and logical instruction of 8085 microprocessor in detail. (CO3) 10
- 6-b. Draw and explain the timing diagram of opcode fetch cycle. (CO3) 10

7. Answer any one of the following:-

- 7-a. Explain the different addressing modes of 8051. Give an example for each one of them. (CO4) 10
- 7-b. Explain the various instruction set of 8051. (CO4) 10

8. Answer any one of the following:-

- 8-a. Explain the LCD interfacing with 8051 microcontroller with suitable diagram. (CO5) 10
- 8-b. Explain 8051 serial port programming with examples. (CO5) 10