

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA

(An Autonomous Institute Affiliated to AKTU, Lucknow)

B. Tech

SEM: IV - THEORY EXAMINATION (2023 - 2024)

Subject: Analog Circuit

Time: 3 Hours

Max. Marks: 100

General Instructions:

IMP: Verify that you have received the question paper with the correct course, code, branch etc.

1. This Question paper comprises of **three Sections -A, B, & C**. It consists of Multiple Choice Questions (MCQ's) & Subjective type questions.
2. Maximum marks for each question are indicated on right -hand side of each question.
3. Illustrate your answers with neat sketches wherever necessary.
4. Assume suitable data if necessary.
5. Preferably, write the answers in sequential order.
6. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.


SECTION-A

20

1. Attempt all parts:-

- 1-a. The unwanted characteristics of amplifier output apart from the desired output is collectively termed as _____(CO1) 1
- (a) Inefficiency
 - (b) Damage
 - (c) Fault
 - (d) Distortion
- 1-b. The distortion is..... in the negative feedback amplifier. (CO1) 1
- (a) constant
 - (b) increses
 - (c) decreases
 - (d) increases or decreases
- 1-c. In the common-mode (CO2) 1
- (a) both inputs are grounded
 - (b) the outputs are connected together
 - (c) an identical signal appears on both inputs
 - (d) the output signals are in-phase
- 1-d. For an Op-amp with negative feedback, the output is (CO2) 1
- (a) equal to the input
 - (b) increased

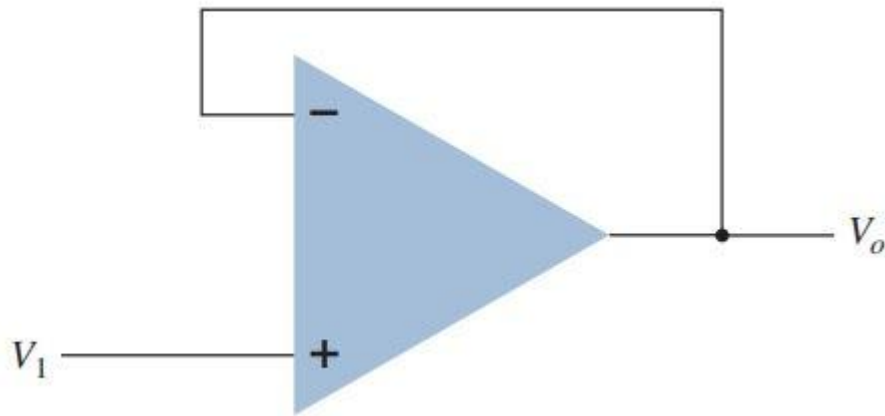- (c) feed back to the inverting input.
- (d) feed back to the noninverting input
- 1-e. Which of the following type of flip-flop is used in 555IC? (CO3) 1
- (a) SR
- (b) D
- (c) T
- (d) JK
- 1-f. Which of the following mode of multi-vibrator does not require trigger to shift to other state? (CO3) 1
- (a) Astable
- (b) Monostable
- (c) Bistable
- (d) None of the mentioned
- 1-g. How many RC sections in RC phase shift oscillator? (CO4) 1
- (a) one
- (b) three
- (c) two
- (d) four
- 1-h. Which of the following is not an example of non-sinusoidal oscillator? (CO4) 1
- (a) Sawtooth Generators
- (b) UJT relaxation oscillator
- (c) Multivibrator
- (d) Colpitts oscillator
- 1-i. The compliance voltage is related to.....(CO5) 1
- (a) oscillators
- (b) current mirrors
- (c) amplifiers
- (d) Power amplifiers
- 1-j. A widlar current source is used (CO5) 1
- (a) to get low value of current
- (b) to get high value of CMRR
- (c) to get low voltage of gain
- (d) to get high value of Output
2. Attempt all parts:-
- 2.a. Write the value of conduction angle of class AB and class C power amplifiers. 2
CO1
- 2.b. What output voltage results in the circuit of figure for $V_1 = 50\text{ V}$? CO2 2



- 2.c. Draw the circuit diagram of full-wave precision rectifier. CO3 2
- 2.d. Write the Barkhausen criterion for sustained oscillations. (CO4) 2
- 2.e. Write the characteristics of current mirrors. (CO5) 2

SECTION-B

30

3. Answer any five of the following:-

- 3-a. Draw and explain the frequency response of CE amplifier. (CO1) 6
- 3-b. Discuss the crossover distortion in class B power amplifier and explain how it can be removed. (CO1). 6
- 3-c. Write the advantages of voltage follower with circuit diagram. (CO2) 6
- 3-d. Compare ideal and practical parameters of Op-amp. (CO2) 6
- 3.e. Draw and explain the integrator circuit with input output waveforms and also write its applications. (CO3) 6
- 3.f. Compare RC and LC oscillators in details. (CO4) 6
- 3.g. Explain the Wilson current mirror and derive the expression of current transfer ratio. (CO5) 6

SECTION-C


50

4. Answer any one of the following:-

- 4-a. Derive the expression of lower and upper cutoff frequencies of n-stage amplifier (multistage amplifier) in terms of single stage amplifier. (CO1) 10
- 4-b. With block diagram explain the advantages and disadvantages of negative feedback amplifier. (CO1) 10

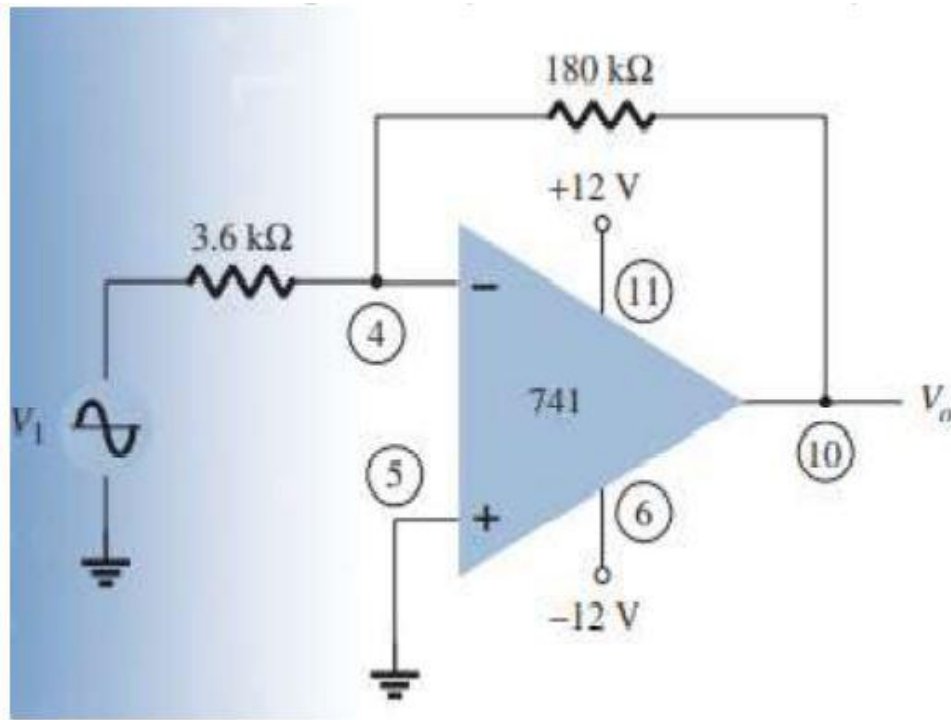5. Answer any one of the following:-

- 5-a. What is virtual ground? Discuss in details the ac parameters of Op-amp. (CO2) 10
- 5-b. Derive the expression of output voltage of a non-inverting amplifier. Also, calculate the output voltage for the circuit of Figure for an input of $V_i = 3.5 \text{ Vrms}$. (CO2) 10



6. Answer any one of the following:-

- 6-a. What is active filters. Derive the expression of cutoff frequency of 2nd order low pass Butterworth filter with circuit diagram. (CO3) 10
- 6-b. Design an astable multi-vibrator using 555 timer for generating a rectangular waveform of frequency of 2 KHz and 60% duty cycle, use $V_{cc} = 12 \text{ V}$. (CO3) 10

7. Answer any one of the following:-

- 7-a. Draw the circuit diagram of a Colpitts Oscillator and explain the principle of operation. (CO4) 10
- 7-b. With a neat diagram explain about Wien Bridge oscillator & derive the expression for frequency of oscillation. (CO4) 10

8. Answer any one of the following:-

- 8-a. In dual input balanced output differential amplifier, transistor Q_1 and Q_2 are biased at $I_{CQ} = 200 \mu\text{A}$ and each transistor has $\beta = 1000$. The differential amplifier is to be designed for $A_d = 180$ and $\text{CMRR} = 80\text{dB}$. Calculate the values of R_C , R_E , R_{id} and R_{ic} . 10
- 8-b. Draw and derive the expression of current transfer ratio of modified current mirror. (CO5) 10