

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA

(An Autonomous Institute)

Affiliated to Dr. A.P.J. Abdul Kalam Technical University, Uttar Pradesh, Lucknow)

B.Tech.

SEM: I - CARRY OVER THEORY EXAMINATION - AUGUST 2022

Subject: Principles of Electrical Engineering

Time: 03:00 Hours

Max. Marks: 50

General Instructions:

1. The question paper comprises three sections, A, B, and C. You are expected to answer them as directed.
2. Section A - Question No- 1 is 1 marker & Question No- 2 carries 2 marks each.
3. Section B - Question No-3 is based on external choice carrying 5 marks each.
4. Section C - Questions No. 4-8 are within unit choice questions carrying 4 marks each.
5. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.

SECTION A

15

1. Attempt all parts:-

- 1.a. Kirchhoff's voltage law is concerned with..... (CO1) 1
- (a) IR drop
  - (b) Battery emfs
  - (c) Both (a)and (b)
  - (d) None of these
- 1.b. Which of the following theorems is applicable for both linear and nonlinear circuits? (CO2) 1
- (a) Superposition
  - (b) Thevenin's
  - (c) Norton's
  - (d) None of these
- 1.c. For getting maximum efficiency from a distributed system the power factor should be..... (CO3) 1
- (a) 1
  - (b) 0.707
  - (c) 0.62

(d) 0.82

- 1.d. Which of the following is not a method of earthing(CO4) 1
- (a) Plate Earthing
  - (b) Pipe Earthing
  - (c) Earthing through Air Medium
  - (d) Rod Earthing
- 1.e. Which one is not essential torque in an indicating instrument? (CO5) 1
- (a) Deflecting torque
  - (b) Controlling torque
  - (c) Damping torque
  - (d) Electrostatic torque

2. Attempt all parts:-


- 2.a. Define source transformation with suitable example.(CO1) 2
- 2.b. State and explain the Superposition theorem. (CO2) 2
- 2.c. Define Band-Width and Quality Factor of series R-L-C circuit. (CO3) 2
- 2.d. What are the features of good conductor in electrical circuit? (C04) 2
- 2.e. What is damping torque in measuring system? (CO5) 2

### SECTION B


15

3. Answer any three of the following:-

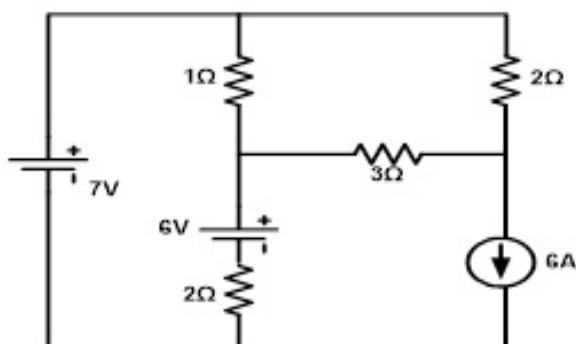- 3.a. Explain KVL and hence find the current in 3 ohm resistance in the given circuit using Mesh Analysis. (CO1) 5



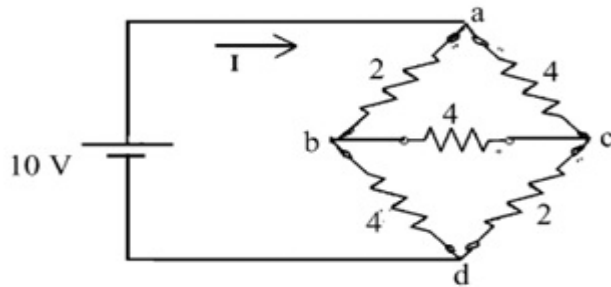- 3.b. Using star-delta transformation, find the current in the branch b-c of the circuit. Consider all the values of resistances are in ohms. (CO2) 5




- 3.c. Two impedances given by  $Z_1 = 5 + j10 \Omega$  and  $Z_2 = 10 - j15 \Omega$ , are connected in parallel. If the total current supplied is 20 A, then find (i) current taken by each branch, (ii) power factor. (CO3) 5
- 3.d. The efficiency of a 400 KVA transformer is 98.77% at full load 0.8 p.f & 99.13% at half load, unity p.f. Find iron & cu loss at both full & half load.(C04) 5
- 3.e. What are safety devices in electrical engineering? Explain SFU,MCB,MCCB and ELCB in details with neat labelled diagram . (CO5) 5

SECTION C


20

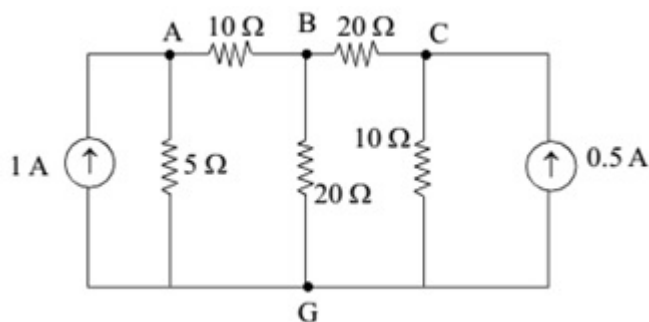4. Answer any one of the following:-

- 4-a. Find the current in  $5 \Omega$  using nodal analysis. (CO1) 4




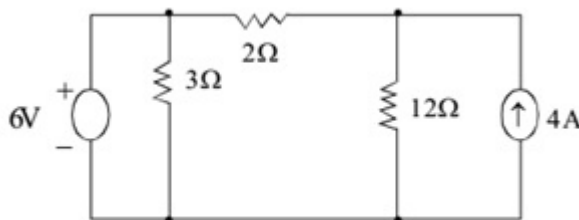- 4-b. Find the current in  $12 \Omega$  resistance using mesh analysis. (CO1) 4



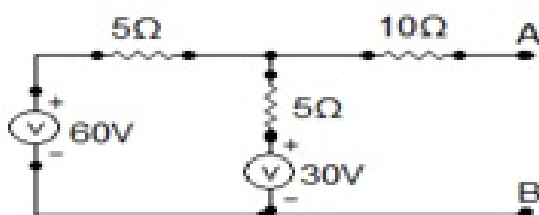5. Answer any one of the following:-

- 5-a. State and prove maximum power transfer theorem. (CO2) 4
- 5-b. Find the Thevenin's equivalent circuit of the given network. (CO2) 4



6. Answer any one of the following:-

6-a. In parallel Resonant circuit (tank circuit) if  $R=50 \text{ ohm}$ ,  $L=0.1\text{H}$  and  $c=140\mu\text{F}$ , Calculate (a)Quality Factor (b) Impedance at resonance (c)Band width (CO3) 4

6-b. Derive the relationship between phase current and line current in 3-  $\phi$  Delta connection. (CO3) 4

7. Answer any one of the following:-

7 Discuss the need of earthing in detail. (C04) 4

7 Explain MCB and MCCB in detail. (C04) 4

8. Answer any one of the following:-

8-a. Explain B-H curve for magnetic materials. (CO5) 4

8-b. Explain different types of sensors. Explain each one giving suitable examples . (CO5) 4