



- (c) 4 NAND gates  
(d) 5 NAND gates
- 1-d. What type of register would have a complete binary number shifted in one bit at a time and have all the stored bits shifted out one at a time? (CO2) 1
- (a) Parallel-in Parallel-out  
(b) Parallel-in Serial-out  
(c) Serial-in Serial-out  
(d) Serial-in Parallel-out
- 1-e. SP stands for \_\_\_\_\_. (CO3) 1
- (a) Stack pointer  
(b) Segment pointer  
(c) Status pointer  
(d) State pointer
- 1-f. What is SIM? (CO3) 1
- (a) Select interrupt mask  
(b) Sorting interrupt mask  
(c) Set interrupt mask  
(d) None of these
- 1-g. Are PUSH and POP instructions are a type of CALL instructions? (CO4) 1
- (a) Yes  
(b) No  
(c) None of the mentioned  
(d) Can't be determined
- 1-h. Which of the ports act as the 16 bit address lines for transferring data through it? (CO4) 1
- (a) PORT 0 and PORT 1  
(b) PORT 1 and PORT 2  
(c) PORT 0 and PORT 2  
(d) PORT 1 and PORT 3
- 1-i. 8-bit ADC will have the step size of \_\_\_\_\_. (CO5) 1
- (a) 19.53 mV  
(b) 4.88 mV  
(c) 1.2 mV

(d) 0.076 mV

- 1-j. Which is true in interfacing 7 segment code display? (CO5) 1
- (a) Transmitted by second port
  - (b) Display is selected by third port
  - (c) Display is selected by second port
  - (d) none of the mentioned

**2. Attempt all parts:-**

- 2.a. Simplify:  $f(A,B,C) = \prod M(1,2,4,6,7)$  using K Map in POS form. (CO1) 2
- 2.b. What do you mean by next state? (CO2) 2
- 2.c. Which interrupt is not level-sensitive in 8085? (CO3) 2
- 2.d. Write registers of 8051. (CO4) 2
- 2.e. Calculate the  $I_{out}$  for binary value 11110000 by assuming  $I_{ref}=2mA$ . (CO5) 2

**SECTION B**

**30**

**3. Answer any five of the following:-**

- 3-a. Simplify:  $f(A,B,C,D) = \sum m(1,2,4,6)$  and implement with logic gates. (CO1) 6
- 3-b.  $F(A,B,C,D) = \sum m(0,5,7,8,9,10,11,14,15)$  minimize the given using K-MAP in SOP form. (CO1) 6
- 3-c. Differentiate between latches & flip flops. (CO2) 6
- 3-d. Design MOD 3 UP/DOWN synchronous counter. (CO2) 6
- 3.e. List the major features of 8085 microprocessor. (CO3) 6
- 3.f. Explain briefly about IE and IP registers. (CO4) 6
- 3.g. Explain different modes of Timer for 8051 microcontroller.(CO5) 6

**SECTION C**

**50**

**4. Answer any one of the following:-**

- 4-a. Find expression for 7 segment LED. (CO1) 10
- 4-b.  $F(A,B,C,D) = \sum m(1,2,3,7,11,15) + \sum d(0,2,5)$  minimize the given using QM method. (CO1) 10

**5. Answer any one of the following:-**

- 5-a. Design a synchronous 3-bit gray code up counter with the help of excitation table. (CO2) 10
- 5-b. i) What is clock? Describe different types of clock. (CO2) 10  
ii) What is the purpose of clock signal?

**6. Answer any one of the following:-**

- 6-a. Explain the direct addressing modes and indirect addressing modes of 8085 with example. (CO3) 10
- 6-b. Explain the functions of the ALE and IO/M' signals of the 8085 microprocessor. (CO3) 10

**7. Answer any one of the following:-**

- 7-a. Mention the advantages of subroutines. Give the range of instructions SJMP, AJMP, LJMP in 8051. (CO4) 10
- 7-b. List out the arithmetic operations of 8051 microcontroller with an example and show how the flags are affected for each operation. (CO4) 10

**8. Answer any one of the following:-**

- 8-a. Explain the LCD interfacing with 8051 microcontroller with suitable diagram. (CO5) 10
- 8-b. What is sensor? Explain various types of sensors. (CO5) 10

2022-23 Jan\_Jun