

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA

(An Autonomous Institute Affiliated to AKTU, Lucknow)

B.Tech

SEM: IV - CARRY OVER THEORY EXAMINATION - SEPTEMBER 2022

Subject: Analog Circuits

Time: 3 Hours

Max. Marks: 100

General Instructions:

1. The question paper comprises three sections, A, B, and C. You are expected to answer them as directed.
2. Section A - Question No- 1 is 1 mark each & Question No- 2 carries 2 mark each.
3. Section B - Question No-3 is based on external choice carrying 6 marks each.
4. Section C - Questions No. 4-8 are within unit choice questions carrying 10 marks each.
5. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.

SECTION A

20

1. Attempt all parts:-

1 What is the output of a class B amplifier for sinusoidal input? (CO1) 1

Question Instruction

4

- (a) Sinusoidal amplifier
- (b) Half-sinusoidal
- (c) Sinusoidal with higher frequency
- (d) Square wave

1 What is the disadvantage of a class B push-pull amplifier? (CO1) 1

- (a) The efficiency reduces
- (b) The figure of merit increases
- (c) The cross-over distortion occurs
- (d) The Q-power dissipation is very large

1 Op-Amp is abbreviated as _____. (CO2) 1

- (a) Operational Amplifier
- (b) Operand amplitude

(c) Operational amplitude

(d) None of the above

1 Op-Amp hasgain. (CO2) 1

(a) High

(b) low

(c) medium

(d) None of these

1 An Op Amp can be used to generate the waveform having _____shape. (CO3) 1

(a) Square

(b) Pulse

(c) Triangular

(d) All of the mentioned

1 The bandwidth of a band-pass filter is the _____. (CO3) 1

(a) sum of the two cutoff f_c

(b) difference of the two cutoff frequency

(c) lower cutoff frequency

(d) None of these

1 In an LC transistor oscillator, the active device is _____. (CO4) 1

(a) LC tank circuit

(b) Biasing circuit

(c) Transistor

(d) None of the above

1 In a phase shift oscillator, we use RC sections. (CO4) 1

(a) Two

(b) Three

(c) Four

(d) None of the above

1 Constant current source in differential amplifier is also called as _____. (CO5) 1

(a) Current Mirror

(b) Current Source

(c) Current Repeaters

(d) All of the mentioned

- 1 A Current Mirror circuit can be design using_____. (CO5) 1
- (a) BJT
- (b) FET
- (c) MOSFET
- (d) All of the above

2. Attempt all parts:-

- 2.a. What is feedback ? Explain different types of feedback topologies. (CO1) 2
- 2.b. Define CMRR of an Op-Amp and what is its ideal value? (CO2) 2
- 2.c. What are the advantages of active filters over Passive filters? (CO3) 2
- 2.d. What is an Oscillator? (CO4) 2
- 2.e. Draw the simple BJT current mirror circuit. (CO5) 2

SECTION B

30

3. Answer any five of the following:-

- 3 Draw and explain the class B Power amplifier. (CO1) 6
- 3 Prove that the input impedance is decreased in voltage shunt feedback amplifier. (CO1) 6
- 3 What is the difference between Inverting and non-inverting operational amplifier? (CO2) 6
- 3 What are the characteristics of an ideal op-amp? (CO2) 6
- 3.e. Differentiate between the comparator and Schmitt trigger with circuit diagram. (CO3) 6
- 3.f. In a Wien – bridge oscillator , if the value of R is $100\text{ K}\Omega$, and frequency of oscillations is 10 kHz, Find the value of capacitor C. (CO4) 6
- 3.g. Draw the simple BJT current mirror circuit and obtain the expression for current transfer ratio using matched transistors. (CO5) 6

Question Instruction

Attempt all Questions.

SECTION C

50

4. Answer any one of the following:-

- 4 Explain the advantage and disadvantage of negative feedback amplifier. (CO1) 10
- 4 Explain the crossover distortion in class B amplifier and explain how it can be reduced? (CO1) 10

5. Answer any one of the following:-

- 5-a. Define the following electrical parameters: (a) input offset voltage (b) input resistance, 10
(c) CMRR
(d) output voltage swing
(e) slew rate. (CO2)
- 5-b. What is differential gain and common-mode gain of a differential amplifier? (CO2) 10
6. Answer any one of the following:-
- 6-a. Discuss with neat diagram of Schmitt trigger circuit with waveform and write its 10
applications. (CO3)
- 6-b. Draw and explain the logarithmic amplifier with output expression. Also write its 10
applications. (CO3)
7. Answer any one of the following:-
- 7-a. Explain the Operation of RC Phase Shift Oscillator with neat diagram and give the condition 10
for sustained oscillation. (CO4)
- 7-b. Draw the circuit diagram of Wien- bridge oscillator and explain its working. (CO4) 10
8. Answer any one of the following:-
- 8-a. Why current mirror circuit is used? Explain performance parameters of current mirror circuit 10
with its characteristics. (CO5)
- 8-b. Explain the performance parameters of the simple current mirror circuit using BJT and 10
MOSFET with neat circuit diagrams. (CO5)

Question Instruction

Attempt all questions.