

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA
(An Autonomous Institute Affiliated to AKTU, Lucknow)

B.Tech

SEM: IV - THEORY EXAMINATION (2022-2023)

Subject: Analog Circuits

Time: 3 Hours

Max. Marks: 100

General Instructions:

IMP: Verify that you have received the question paper with the correct course, code, branch etc.

1. This Question paper comprises of **three Sections -A, B, & C.** It consists of Multiple Choice Questions (MCQ's) & Subjective type questions.
2. Maximum marks for each question are indicated on right -hand side of each question.
3. Illustrate your answers with neat sketches wherever necessary.
4. Assume suitable data if necessary.
5. Preferably, write the answers in sequential order.
6. No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.

SECTION A

20

1. Attempt all parts:-

- 1-a. Which of the following amplifier is designed to operate in digital pulses? (CO1) 1
- (a) Class D
(b) Class C
(c) Class AB
(d) Class B
- 1-b. Which of the following FETs has the lowest input impedance? (CO1) 1
- (a) JFET
(b) MOSFET depletion-type
(c) MOSFET enhancement-type
(d) None of the above
- 1-c. A certain noninverting amplifier has R_1 of 1 k Ω and R_f of 100 k Ω . The closed-loop voltage gain is (CO2) 1
- (a) 100000
(b) 1000

- (c) 101
(d) 100
- 1-d. The two modes of operation of op-amp are _____. (CO2) 1
 (a) Differential and Common Mode
 (b) Differential and Inverting Mode
 (c) Non-inverting and Inverting Mode
 (d) None of these
- 1-e. The output of a Schmitt trigger is a (CO3) 1
 (a) pulse waveform.
 (b) sawtooth waveform.
 (c) sinusoidal waveform.
 (d) triangle waveform
- 1-f. Voltage drop across Superdiode is _____. (CO3) 1
 (a) 0.6 V
 (b) 0.7 V
 (c) 0V
 (d) infinite
- 1-g. If Barkhausen criterion is not satisfied by an oscillator circuit, it will (CO4) 1
 (a) Using only a series tuned circuit as a load on the amplifier
 (b) Providing adequate positive feedback
 (c) Phase shifting the output by 180° and feeding this output to the input
 (d) None of the above
- 1-h. Quartz crystal is most commonly used in crystal oscillators because (CO4) 1
 (a) It has superior electrical properties
 (b) It is easily available
 (c) It is quite inexpensive
 (d) None of the above
- 1-i. The current source which has a very high output resistance? (CO5) 1
 (a) Simple current mirror
 (b) Wilson current mirror
 (c) Widlar current mirror
 (d) All of the mentioned

- 1-j. When the two input terminals of a differential amplifier are grounded (CO5) 1
- (a) the base currents are equal.
 - (b) the collector currents are equal.
 - (c) an output error voltage usually exists.
 - (d) the ac output voltage is zero.

2. Attempt all parts:-


- 2.a. Why gain of amplifier is reduced at lower and higher frequencies? (CO1) 2
- 2.b. Draw and explain close loop inverting Op-Amp amplifier. (CO2) 2
- 2.c. Draw the block diagram of IC 555 Timer. (CO3) 2
- 2.d. Give the comparison between RC and LC oscillators. (CO4) 2
- 2.e. What are the possible sources of error in the current mirrors? (CO5) 2

SECTION B

30

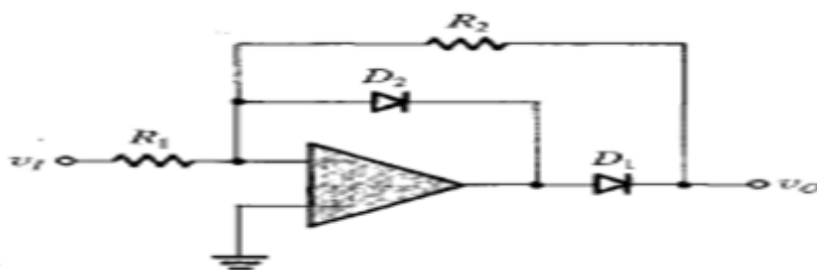3. Answer any five of the following:-

- 3-a. Prove that the closed-loop gain is reduced in the current series feedback amplifier. (CO1) 6
- 3-b. Draw and explain the frequency response of CS/CE amplifier. (CO1) 6
- 3-c. Explain why proper interpretation of op-amp data sheets is important. (CO2) 6
- 3-d. What information is contained in the typical op-amp data sheet? (CO2) 6
- 3.e. Consider the circuit in Fig. with $R_x = 1 \text{ k}\Omega$ and $R_2 = 10 \text{ k}\Omega$. Find v_0 and the voltage at the amplifier output for $v_i = +1 \text{ V}$, -10 mV , and -1 V . Assume the op amp to be ideal with saturation voltages of $\pm 12 \text{ V}$. The diodes have 0.7 V voltage drops at 1 mA , and the voltage drop changes by 0.1 V per decade of current change. (CO3) 6



- 3.f. Explain the principle of operation of clapp oscillator. (CO4) 6
- 3.g. For an Op-Amp having a slew rate of $SR = 2 \text{ V/s}$, what is the maximum closed-loop voltage gain that can be used when the input signal varies by 0.5 V in 10 s ? (CO5) 6

SECTION C


50

4. Answer any one of the following:-

- 4-a. Determine the voltage gain, input and output impedance with feedback for voltage series feedback having $A = -100$, $R_i = 10\text{ kohm}$, $R_o = 20\text{ kohm}$ for feedback of (a) $\beta = -0.1$ (b) $\beta = 0.5$. (CO1) 10
- 4-b. Explain and derive the effective bandwidth of an n-stage Cascaded amplifier? (CO1) 10

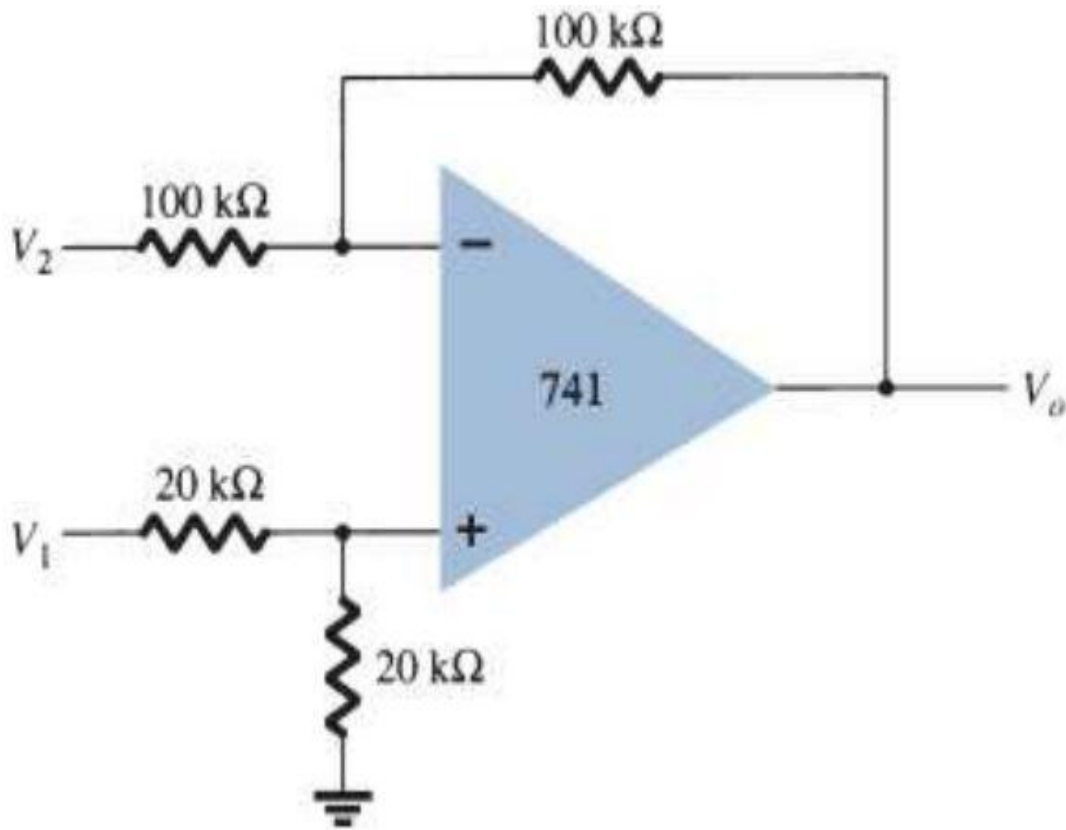5. Answer any one of the following:-

- 5-a. Determine the gain and bandwidth of a CE Amplifier from its frequency response curve. (CO2) 10
- 5-b. Determine the output voltage for the circuit of fig. $V_1 = 5\text{ Volt}$ and $V_2 = 10\text{ Volt}$. (CO2) 10



6. Answer any one of the following:-

- 6-a. A Schmitt trigger with the upper threshold level $V_{UT} = 0\text{ V}$ and hysteresis width is 0.2 V convert 1 KHz sine wave of 4 Vpp into a square wave. Calculate the time duration of the negative and positive portion of the output waveform. (CO3) 10
- 6-b. Design a first-order bandpass filter for the following specification; Cut off frequency, $f_L = 100\text{ Hz}$, $f_H = 500\text{ Hz}$, and $A = 5$. Also, draw Gain Vs Frequency response curve. (CO3) 10

7. Answer any one of the following:-

- 7-a. Sketch the circuit of a phase shift oscillator and explain its design approach. 10
What are the factors which affect the frequency stability of an oscillator? (CO4)
- 7-b. Explain the drawback of Colpitt oscillator and how it is overcome in Clapp oscillator. (CO4) 10

8. Answer any one of the following:-

- 8-a. Explain in detail how we can improve the performance of current mirror circuits of various types. (CO5) 10
- 8-b. Describe what happens to each of the output voltages (V_{out1} and V_{out2}) as the input voltage (V_{in}) decreases: (CO5) 10

